 



# Single Cycle CPU

Chris Nevison, Colgate University


(with minor modifications by Alyce Brady, Kalamazoo College)



 
**Register File: Read 2 Registers Simultaneously**



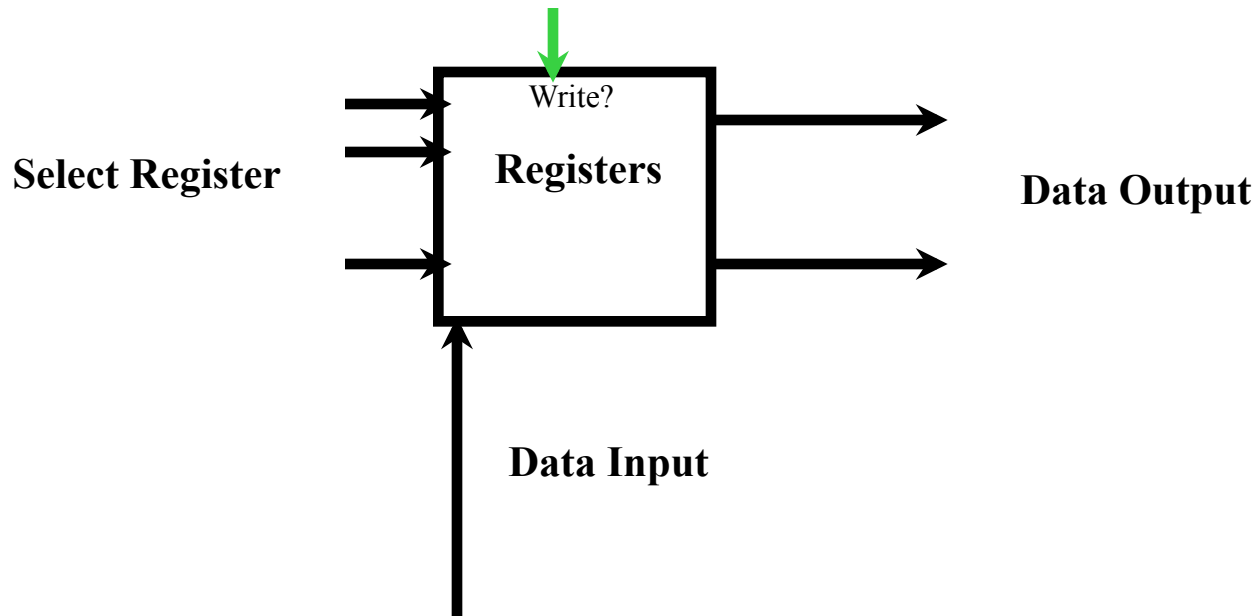**Register File: Read 2 and Write 1 Simultaneously**




One Step Back

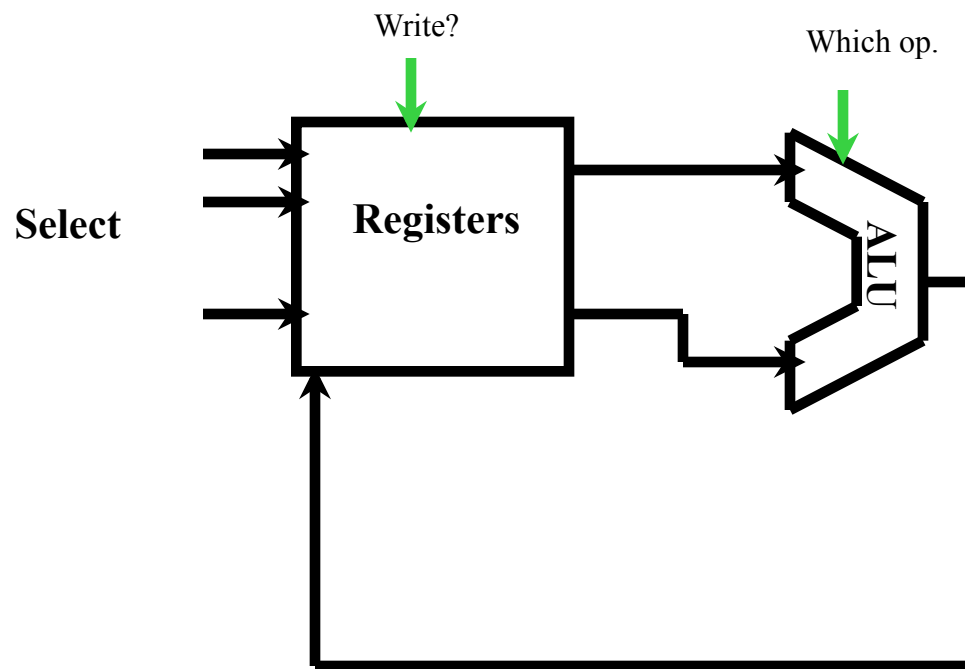


R-Type Instruction Path

e.g., `add $t0, $t1, $t2`

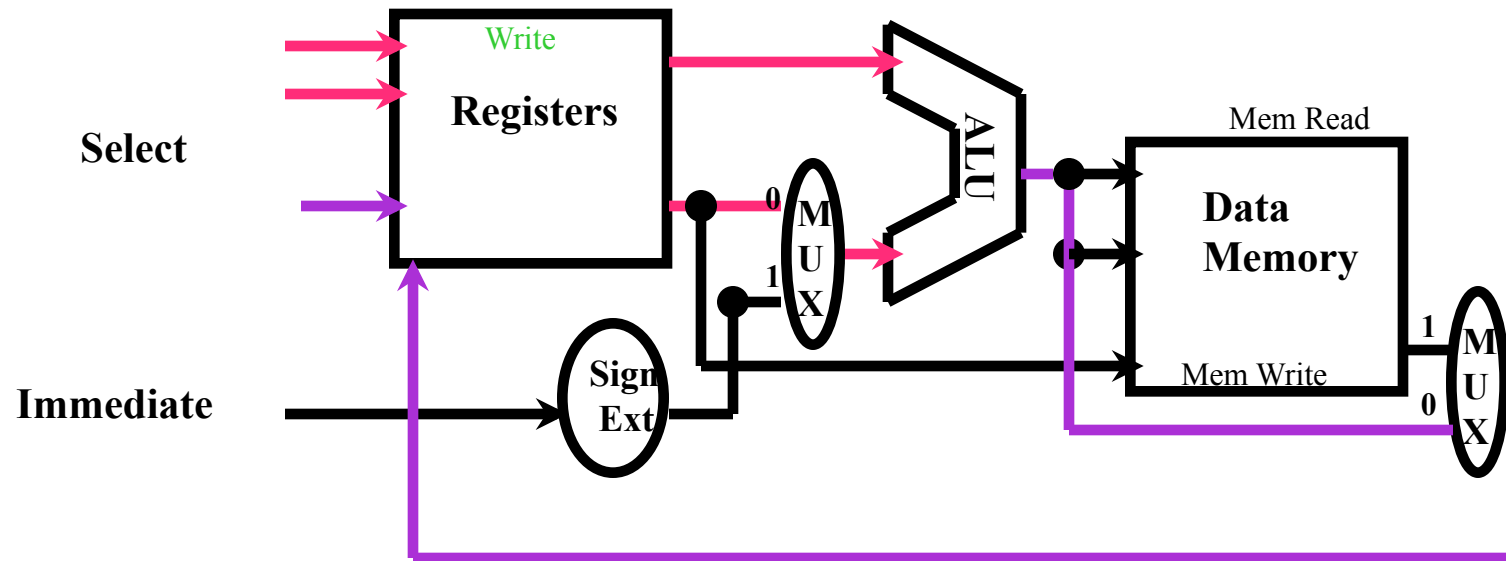


R-Type Instruction Path (in a larger context)

e.g., add \$t0, \$t1, \$t2

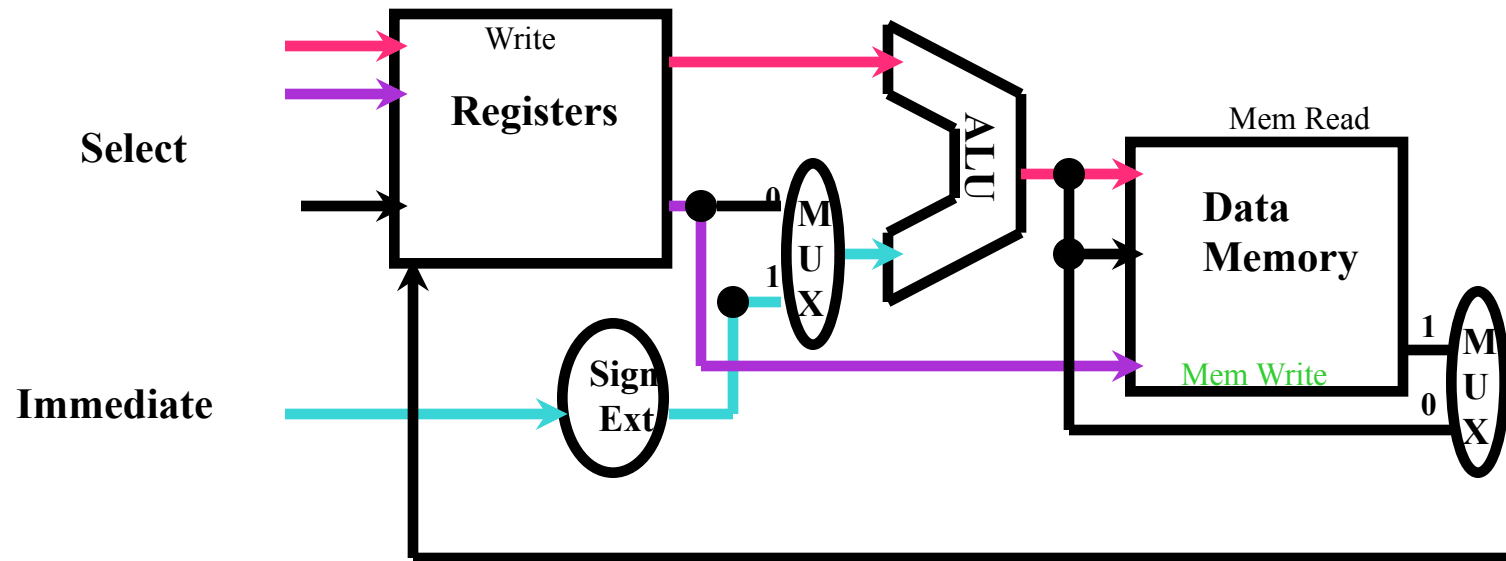

Load/Store Instruction Path


e.g., `sw $t0, 100($s0)`

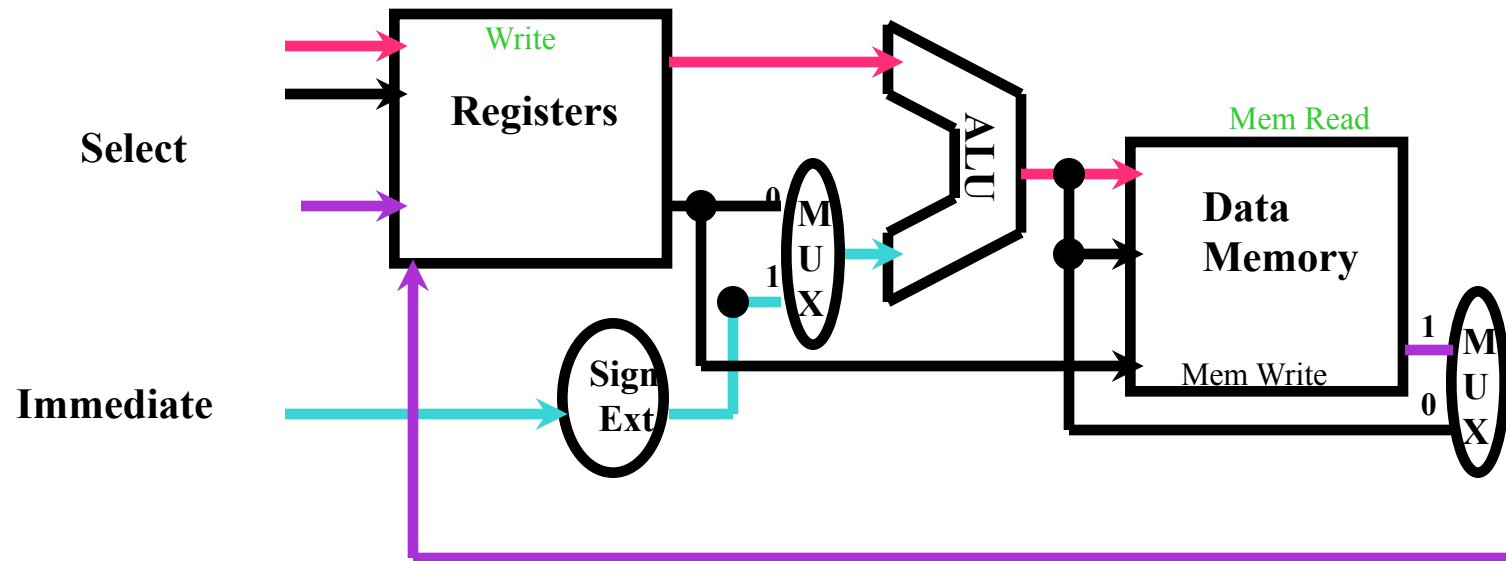

Load/Store Instruction Path


e.g., `lw $t0, 100($s0)`




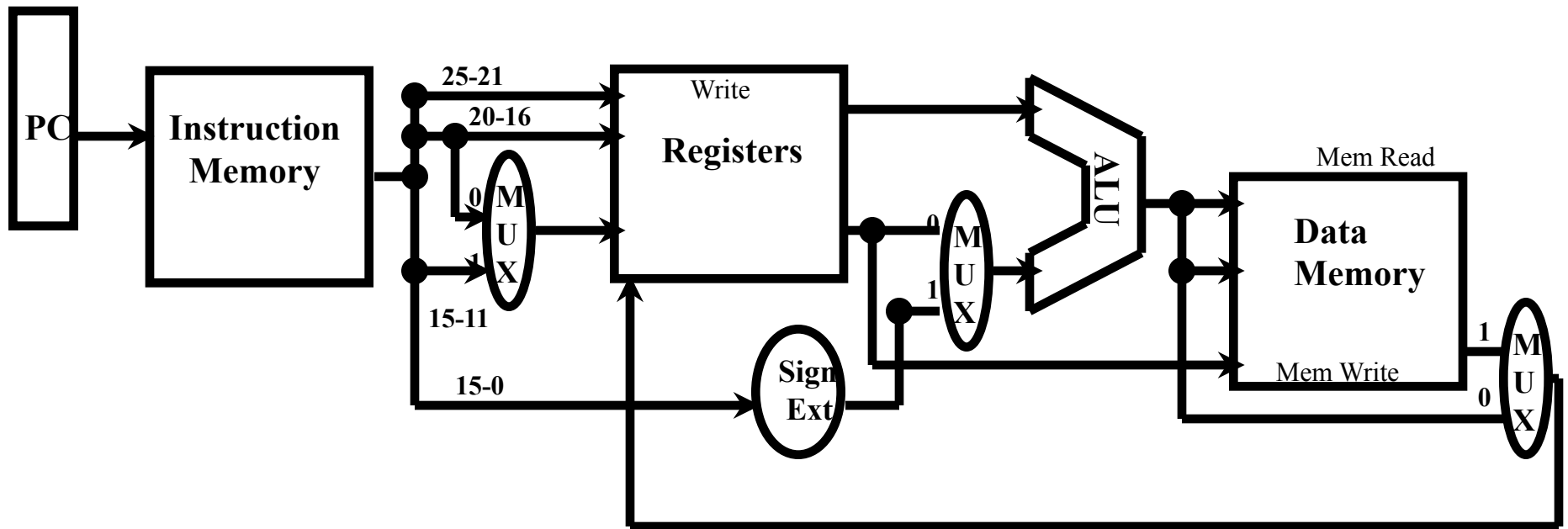

Instruction Path with Instruction from Memory

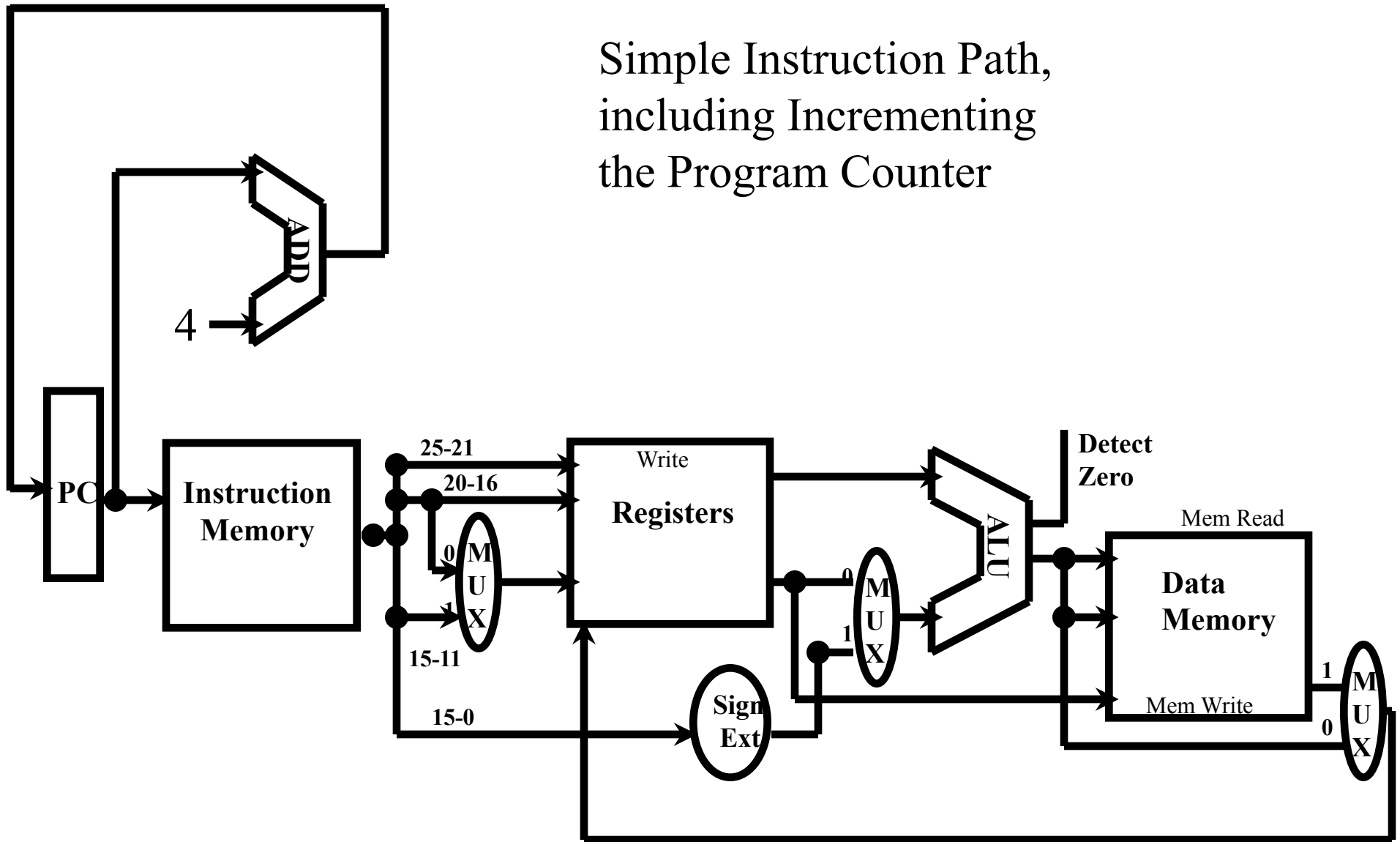Simple Instruction Path,  
including Incrementing  
the Program Counter




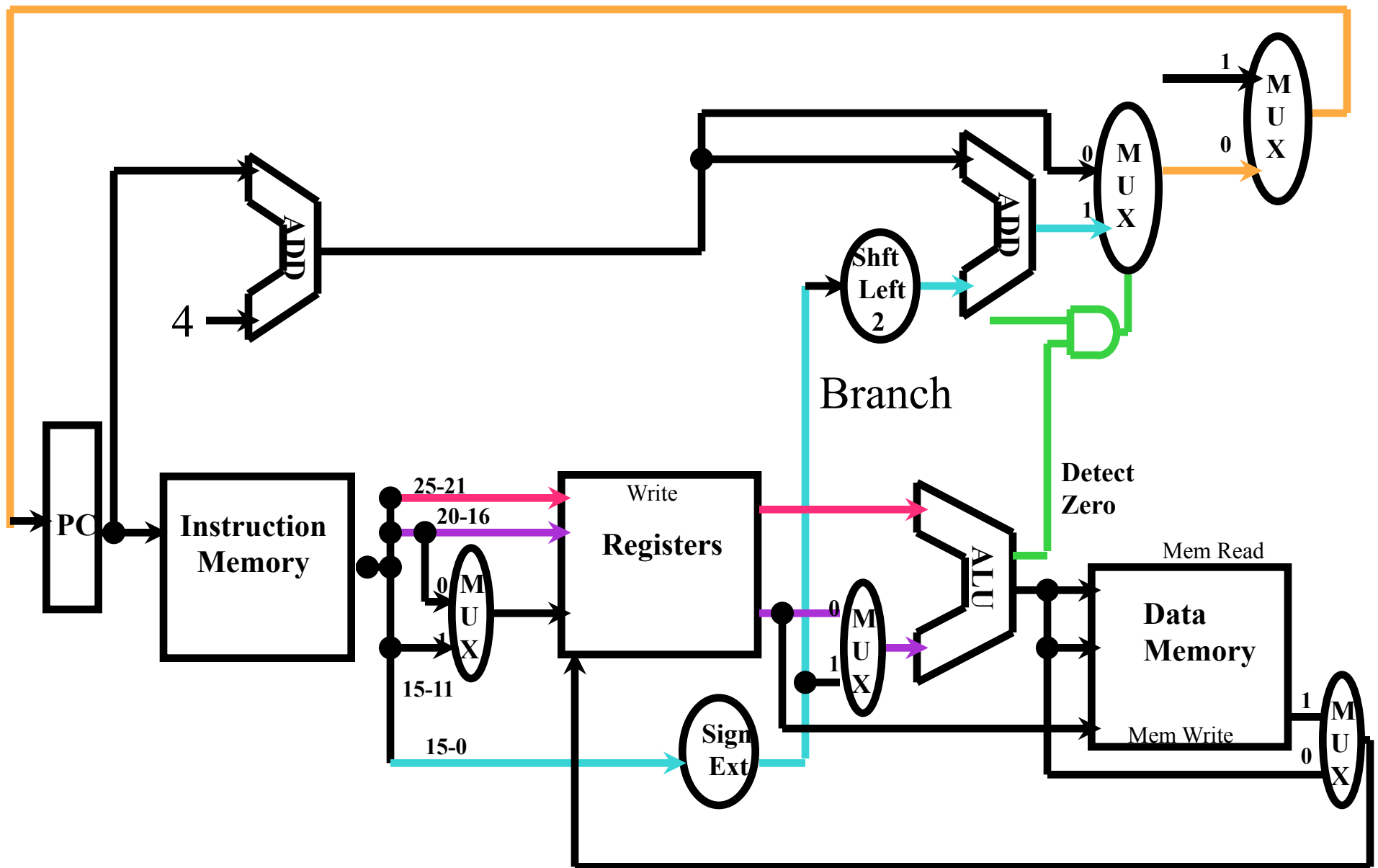


Branch Instruction Path

e.g., beq \$s0, \$zero, addr



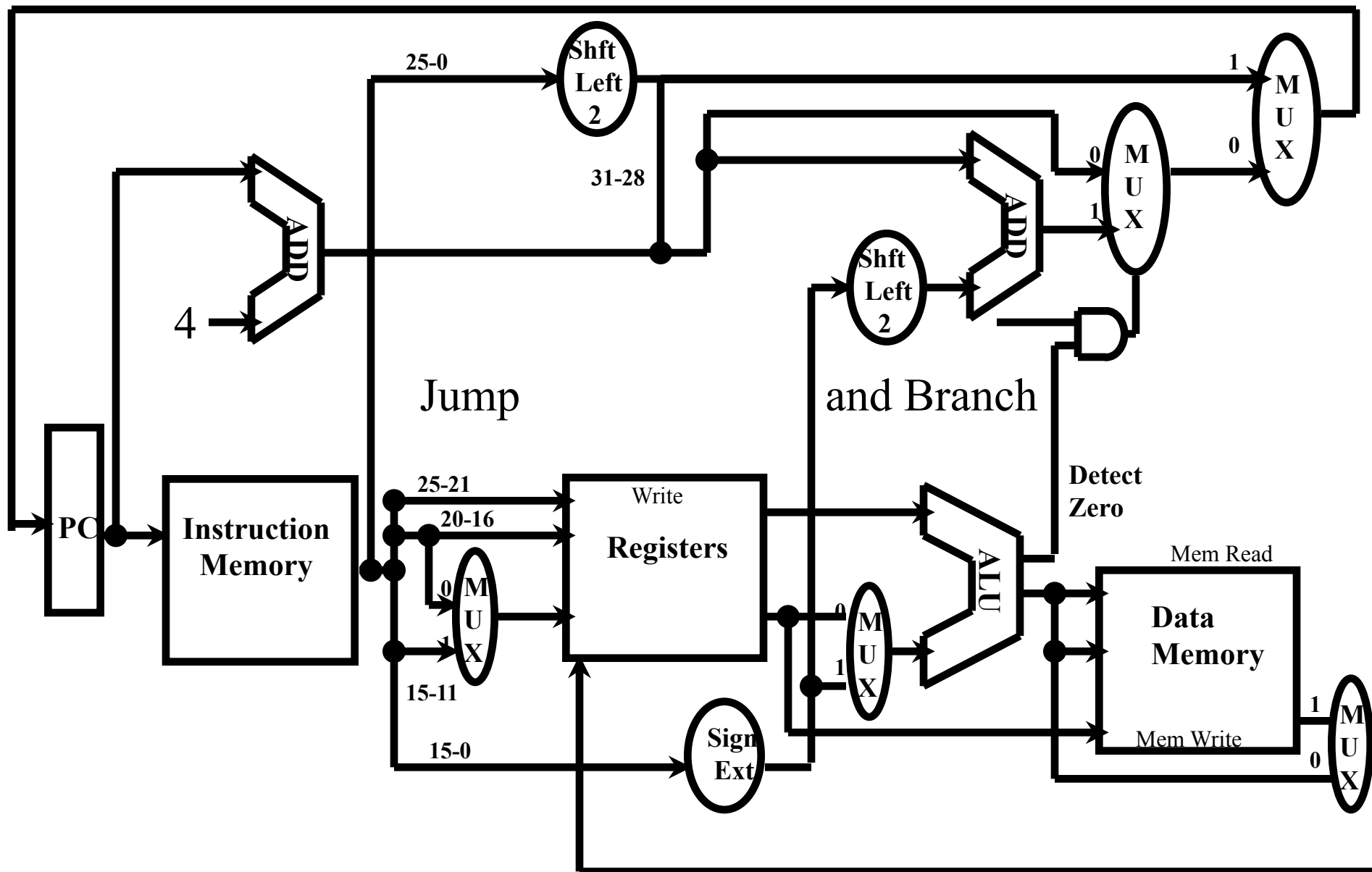

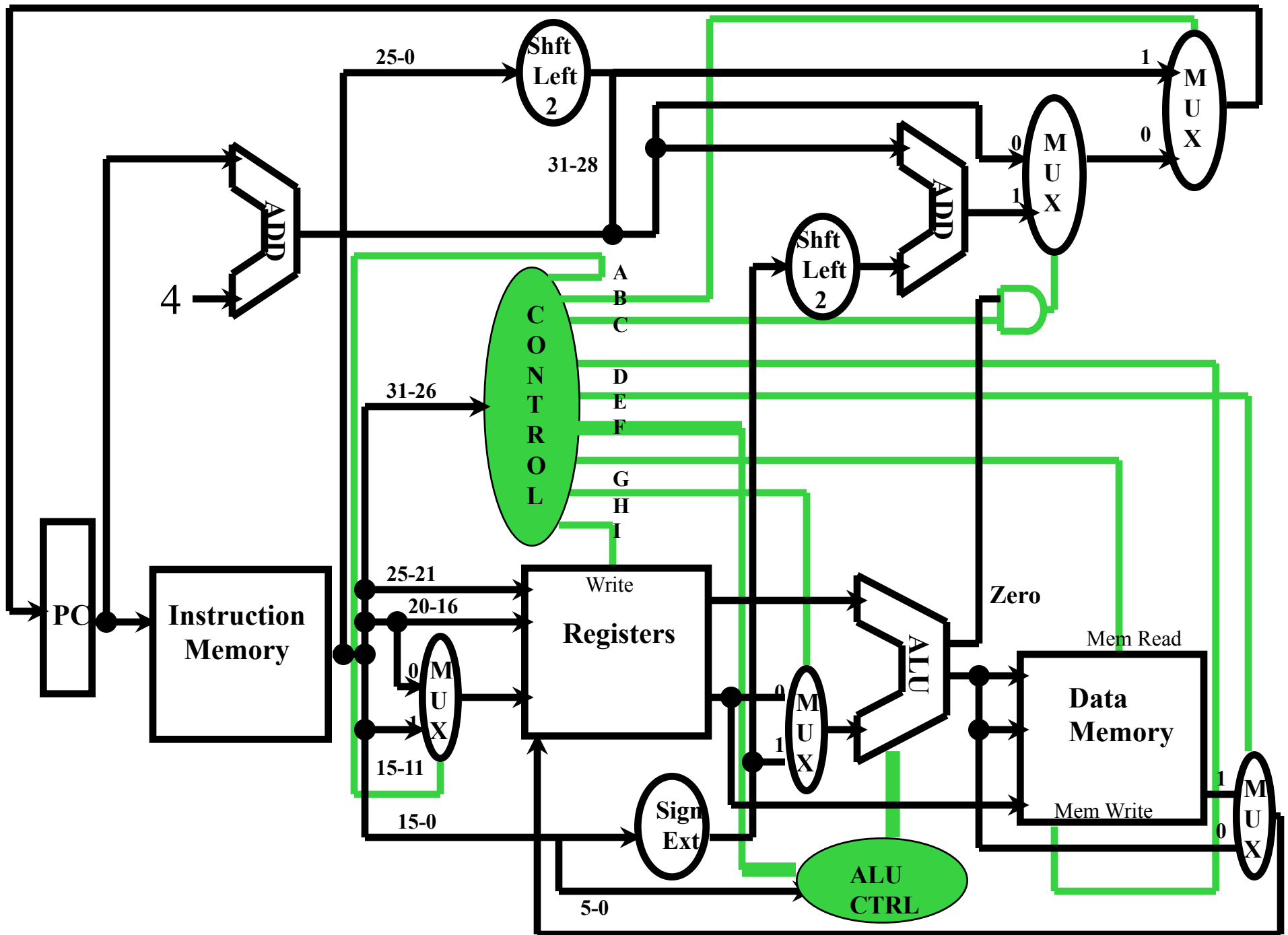




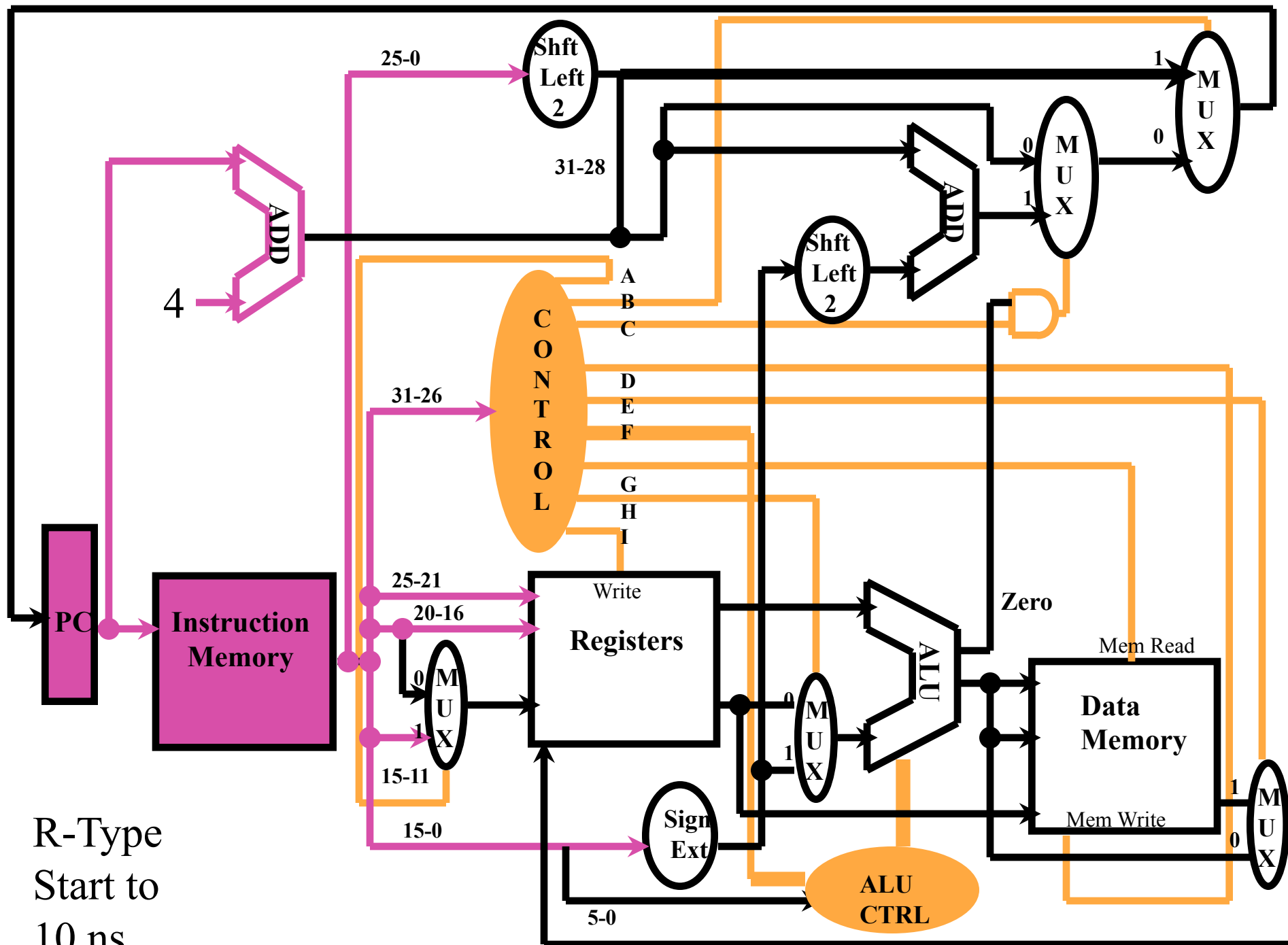
# Control Lines, Top to Bottom

- A RegDst
- B Jump
- C Branch
- D MemWrite
- E MemToReg
- F ALUOp
- G MemRead
- H ALUSrc
- I RegWrite







R-Type  
Start to  
10 ns

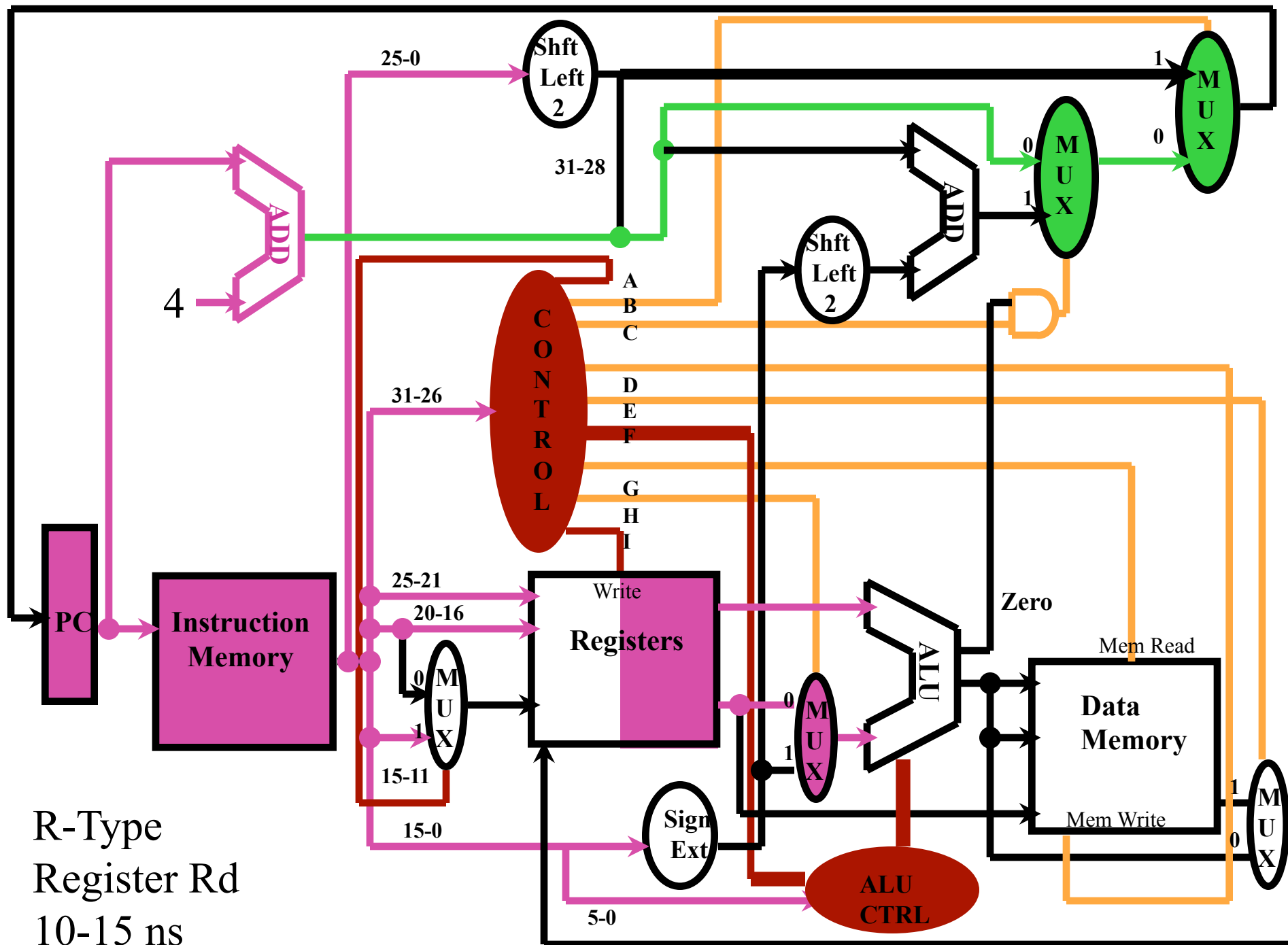



R-Type  
Register Rd  
10-15 ns

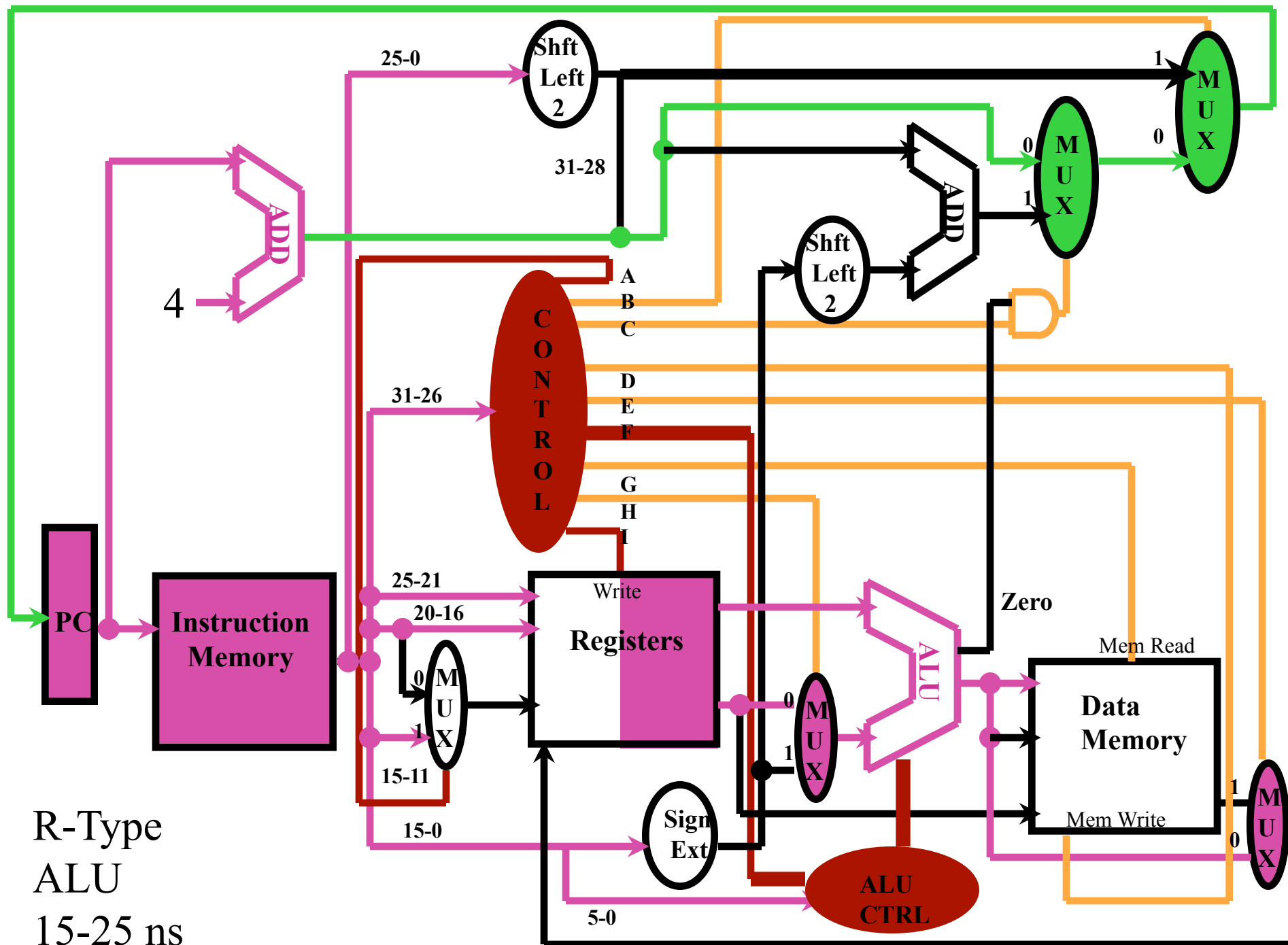


R-Type  
ALU  
15-25 ns

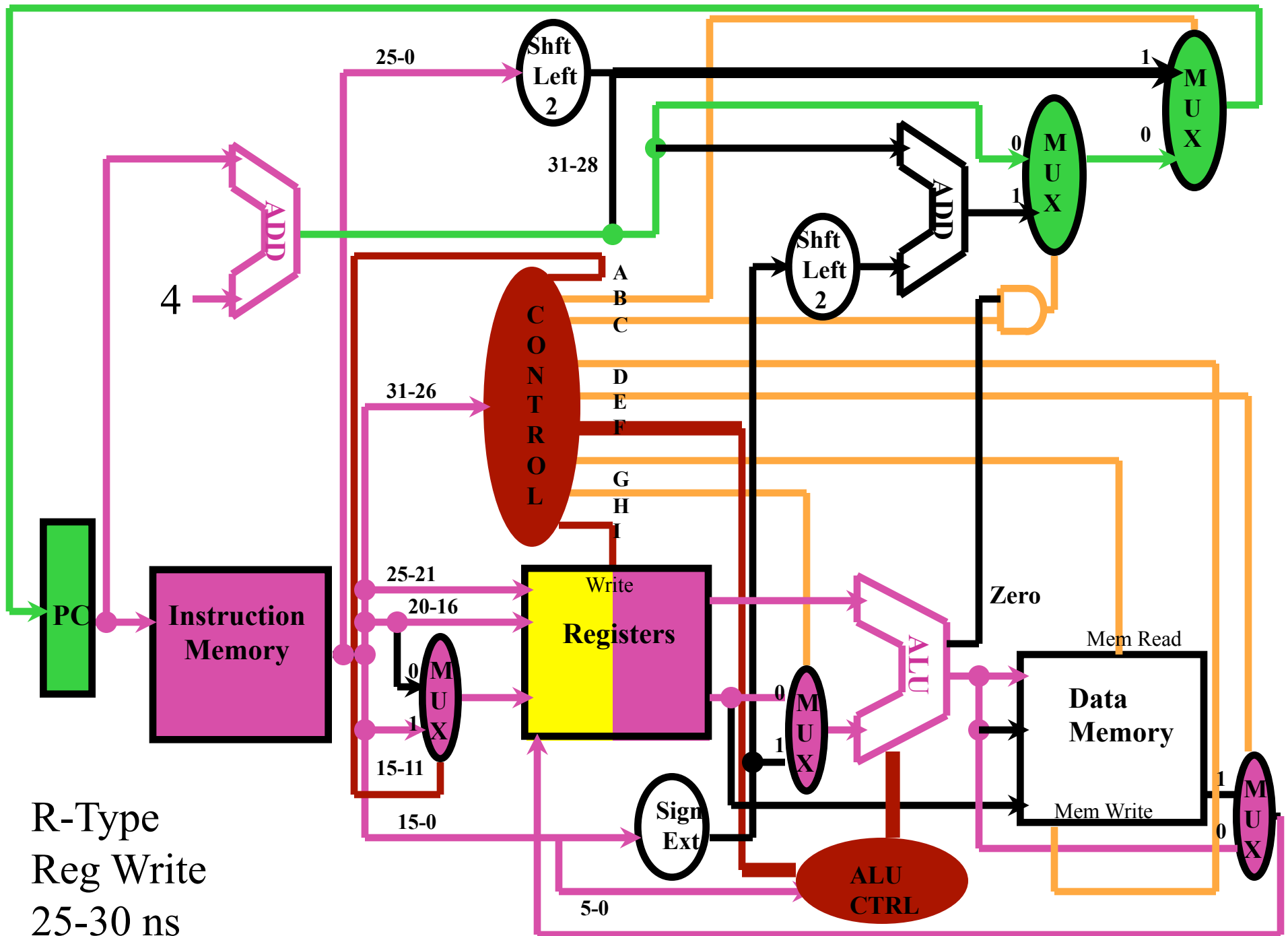


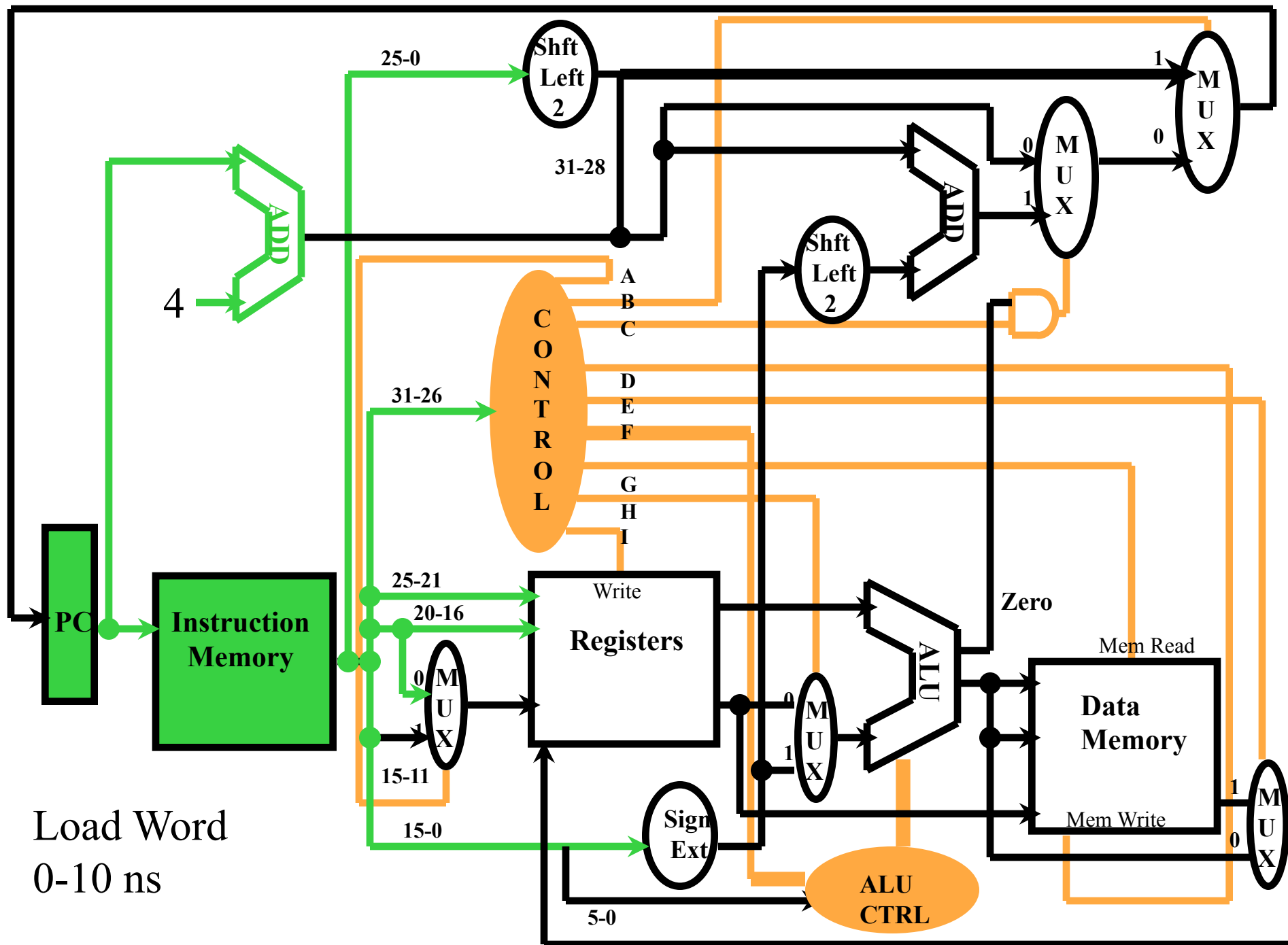

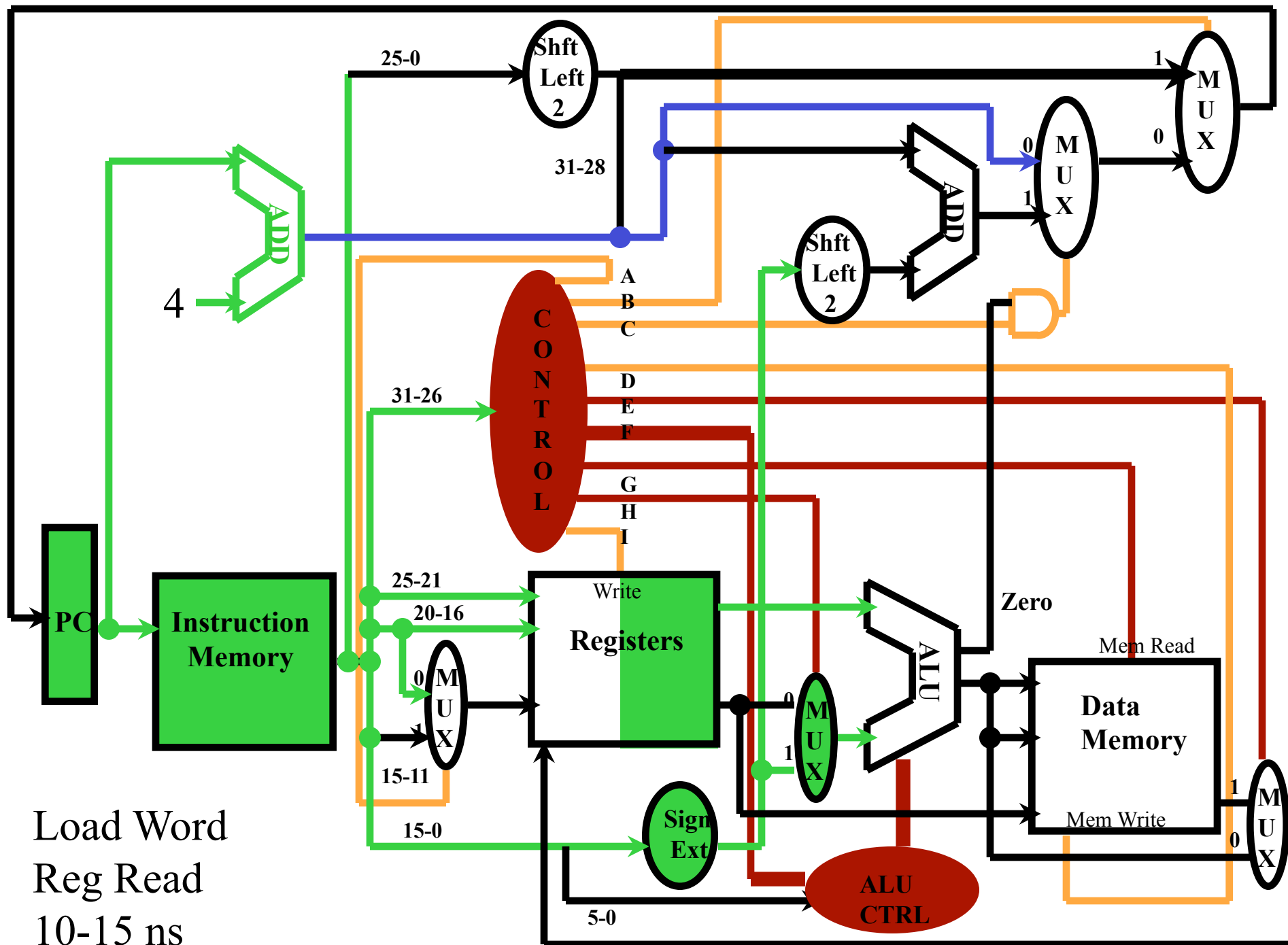


Load Word  
Reg Read  
10-15 ns

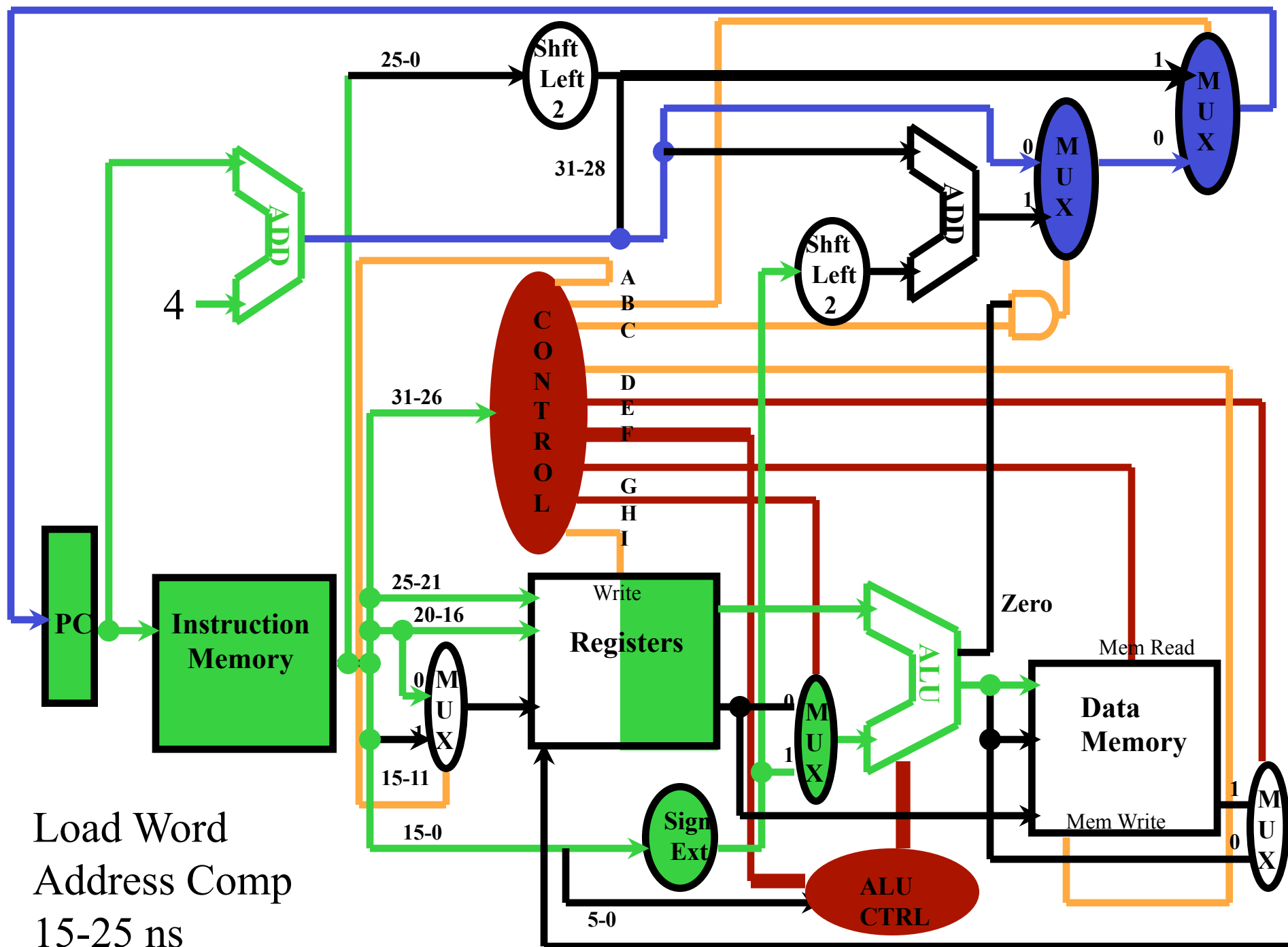


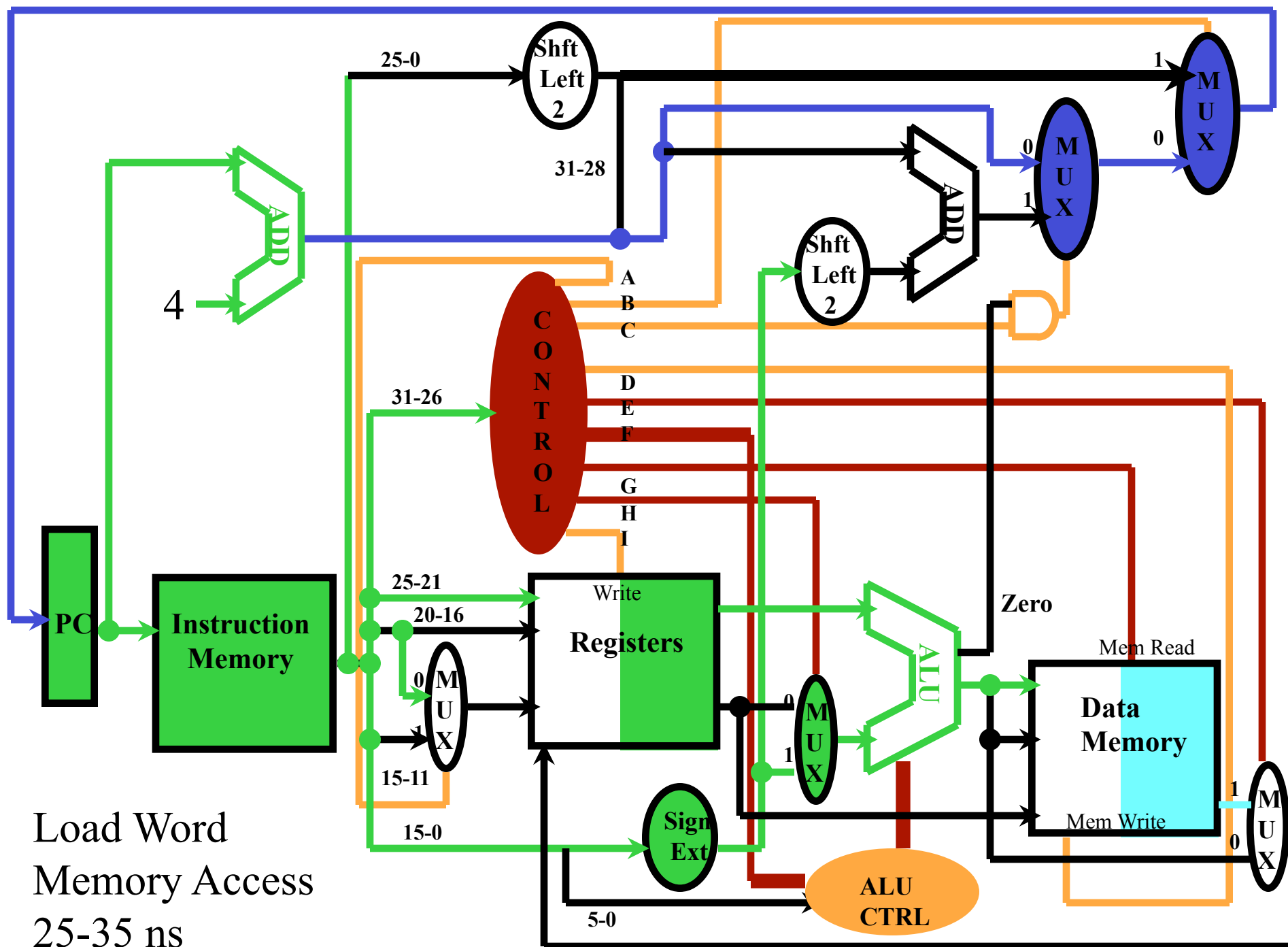





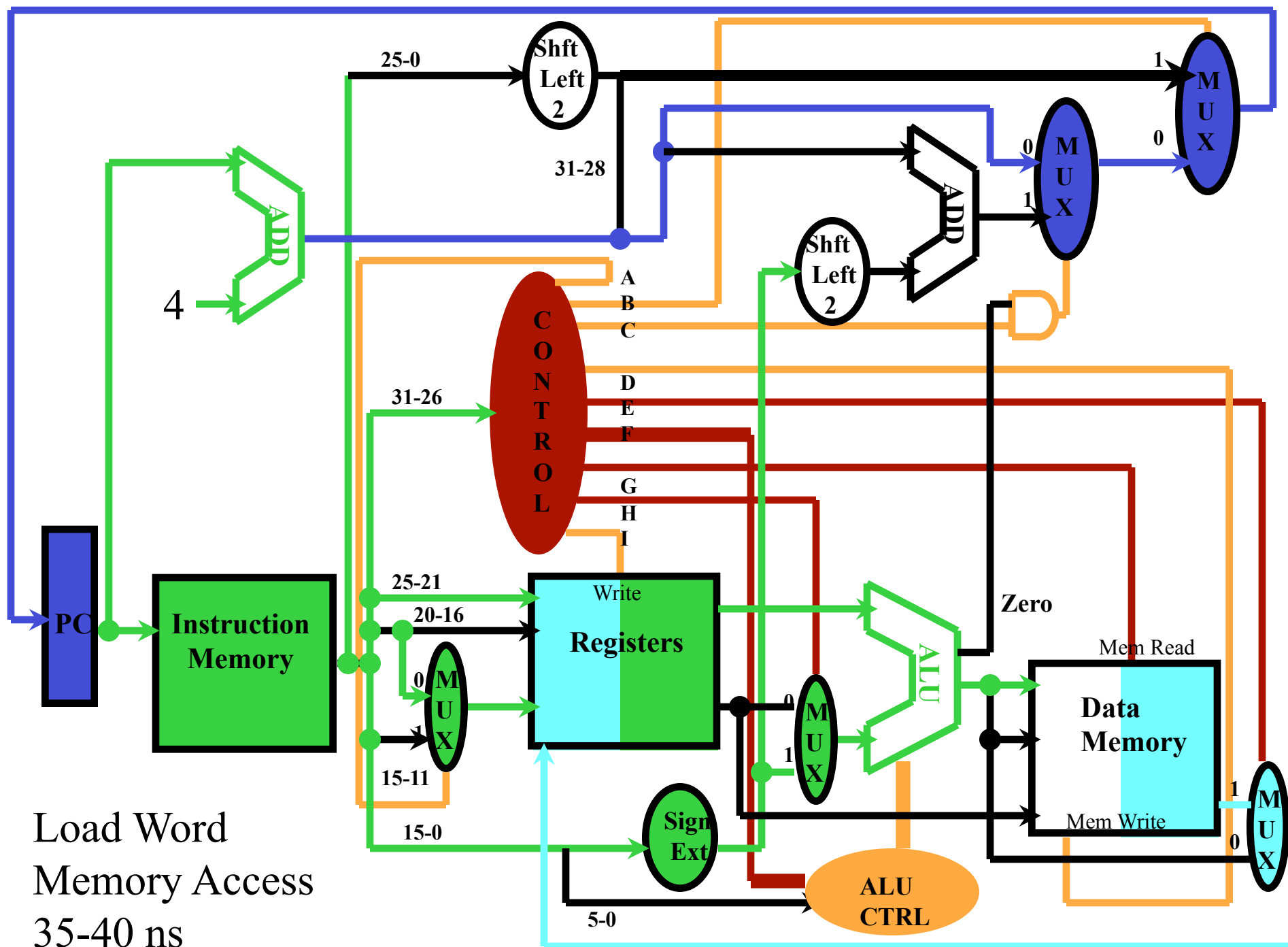

Load Word  
Memory Access  
35-40 ns

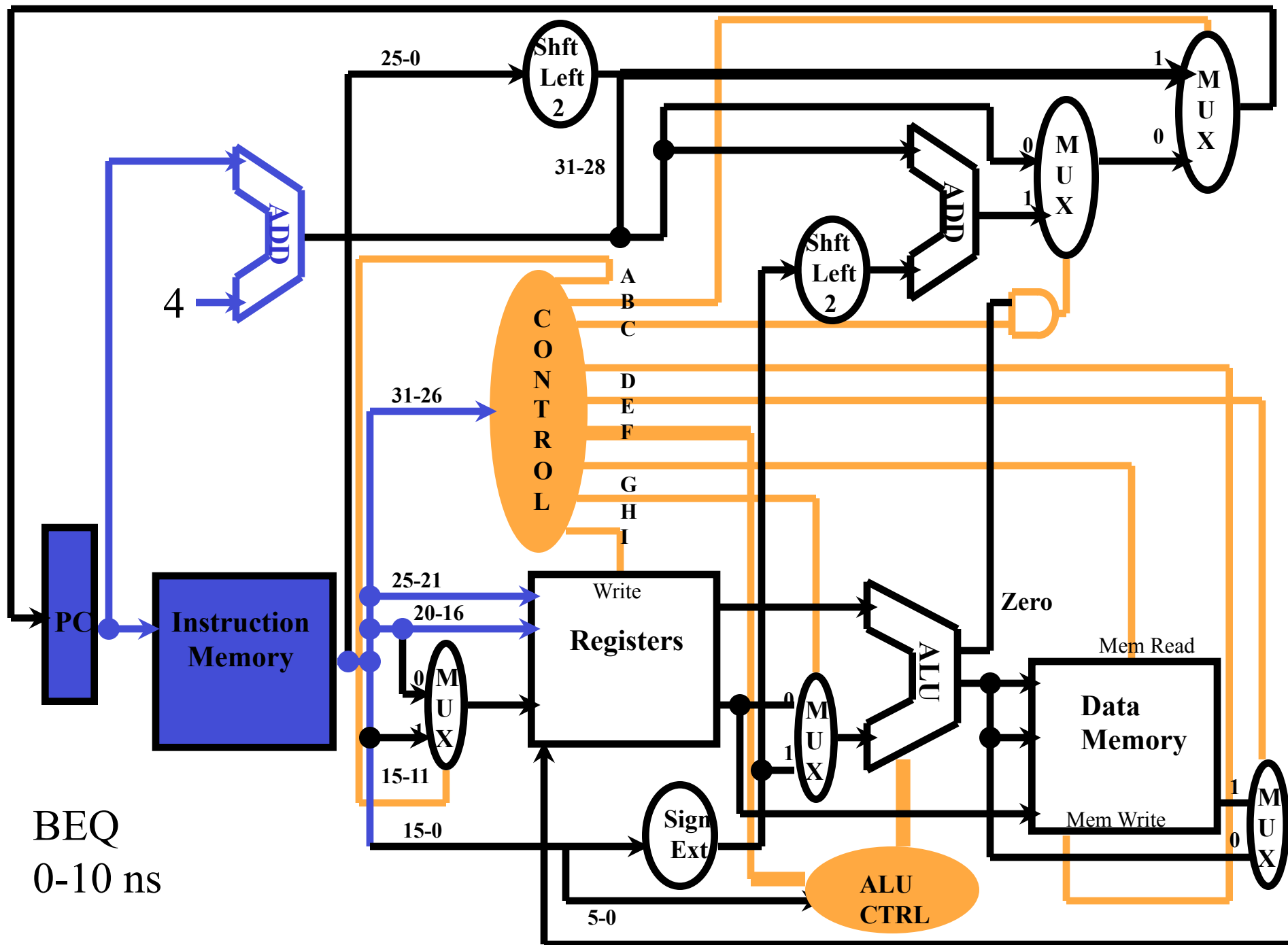

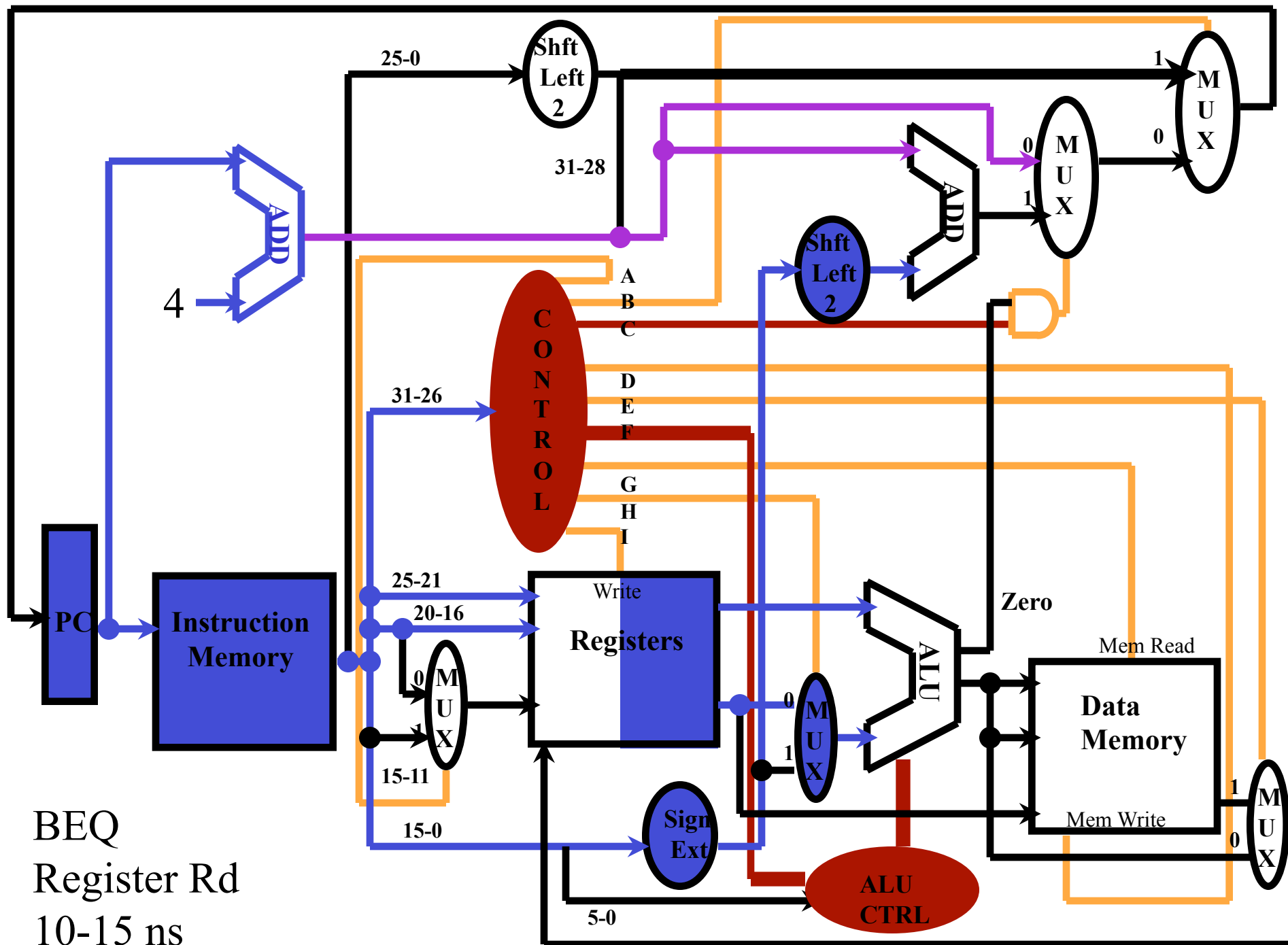

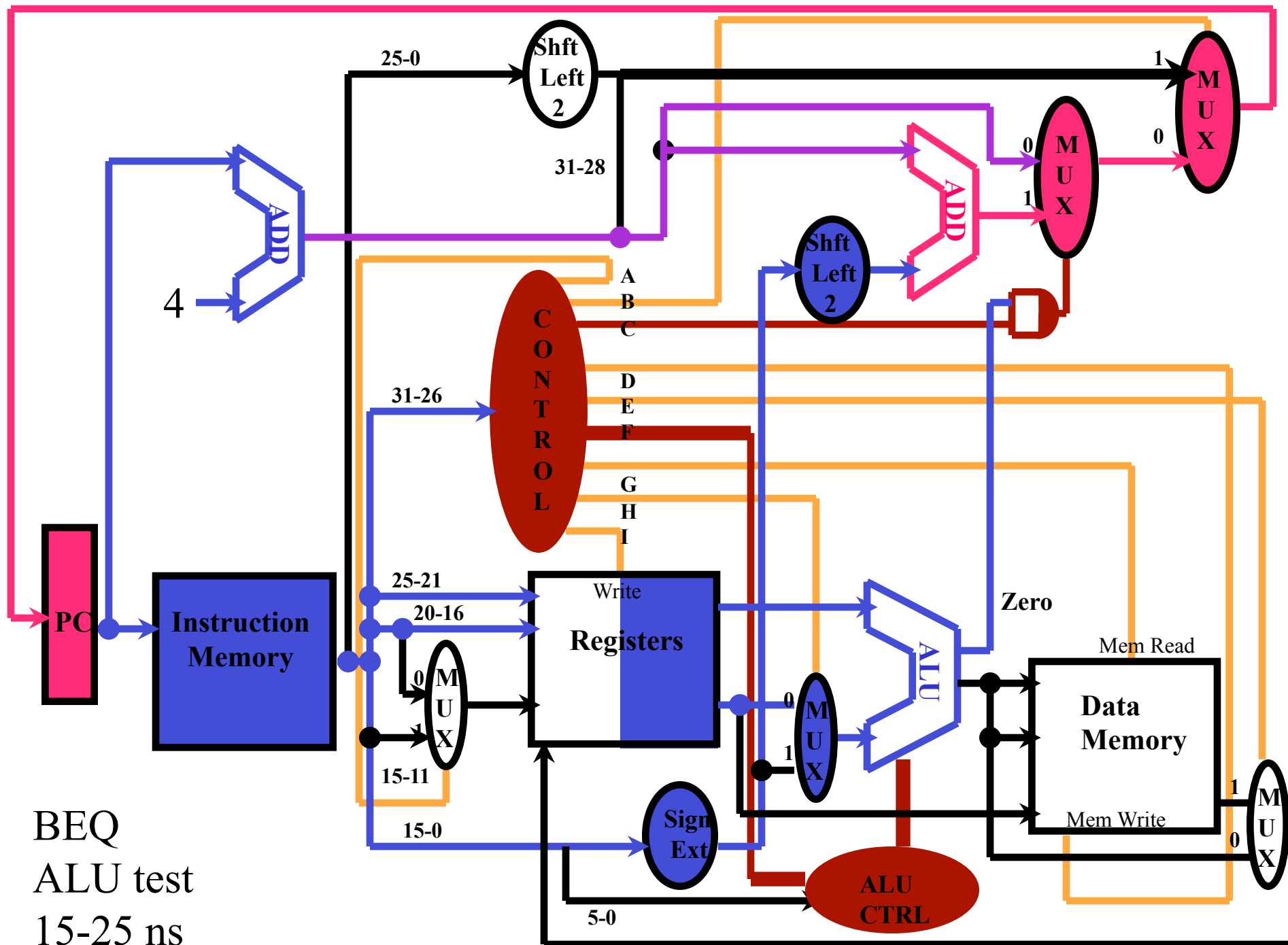

BEQ  
ALU test  
15-25 ns